

1. Use Composer and Hspice to simulate the differential pair as shown at Fig.1 with  $V_{DD}=1.8V$ . (30%)
  - (a) Design a differential pair with gain  $A_{DM} > 5$  and  $A_{CM} < 0.04$  for both input common mode voltage = 0.6 and 1.8. (20%)
  - (b) Simulate the frequency response of  $A_{DM}$  when input common mode voltage=1V, and base on the simulation parameter of .lis file to calculate dominant pole. (5%)
  - (c) Simulate the frequency response of  $A_{CM}$  when input common mode voltage=1V, and identify what makes the  $A_{CM}$  deteriorate at the high frequency. (5%)

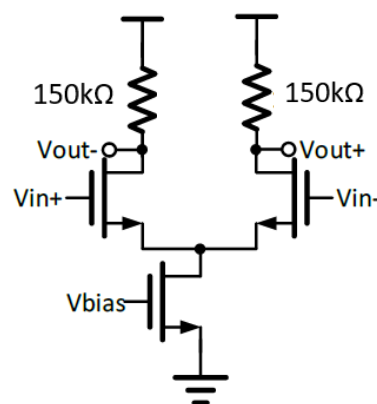


Fig. 1.

2. Design a **1:5** wide-swing cascode current source as shown in Fig. 2(a) with  $V_{DD}=1.8V$ . (40%)
  - (a) With  $I_{ref} = 20\mu A$  ( $I_{out} = 100\mu A$ ), design the W/L sizes of  $M_1 \sim M_4$ , and the dc bias  $V_b$  to get  $R_{out} > 500k\Omega$  when  $V_{out} = 250mV$ . (20%)
  - (b) Use the circuit structure as shown in Fig. 2(b) as a reference to design a bias generation circuit of  $V_b$  with  $I_{in} = 20\mu A$  ( $I_{out} = 100\mu A$ ). State the  $M_5$ 's and  $M_6$ 's (Fig. 2. (b)) design strategy and show in hand calculation. And express  $V_{in1}$ ,  $V_{in2}$ , and  $V_{out}$  in terms of  $V_{ov}$  and  $V_{th}$ . (20%)

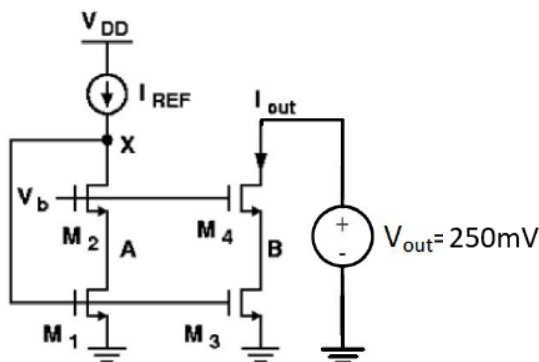


Fig. 2.(a)

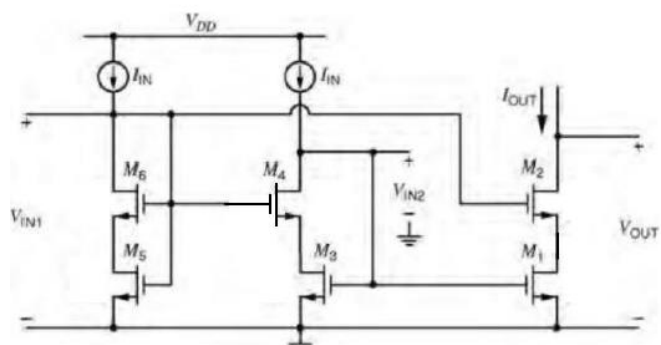


Fig. 2.(b)

3. Use Composer and Hspice to simulate the common source and source follower as shown in Fig. 3 with  $V_{dd}=1.8V$ . Every single one of MOS's  $c_{gtot}$ ,  $c_{stot}$ ,  $c_{dtot}$ , and  $c_{btot}$  can't have more than 70fF under your design. (30%)

☆ *Before you start to simulate the .ac noise*

1. Find the title "Flicker and Thermal noise Model Parameters" in "cic018.l".

2. Use the "replace all" to change value of the parameter into  $KF=1E-29$ .

3. Hint: use ".noise V(vout) vin 10000"

- (a) Design a common source with gain  $A_1 > 50$  and plot the output noise's spectrum as shown in Fig.3. (a). Identify the corner frequency and pole of thermal noise. (6%)
- (b) Design a source follower with gain  $A_2 > 0.7$  and plot the output noise's spectrum as shown in Fig. 3. (b). Identify the corner frequency and pole of thermal noise. (6%)
- (c) Compare between (a) and (b). Which one has higher output flicker noise? Which one has higher thermal noise's pole? Why? (6%)
- (d) Find the output thermal noise of CS and SF. Which one is bigger? Why? (6%)
- (e) Find the input referred thermal noise of CS and SF. Which one is bigger? Why? (6%)

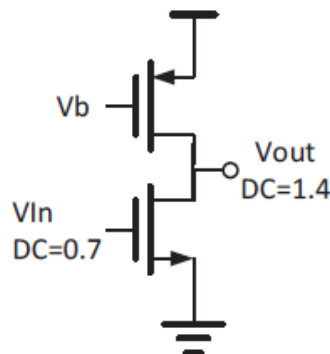


Fig.3 (a)

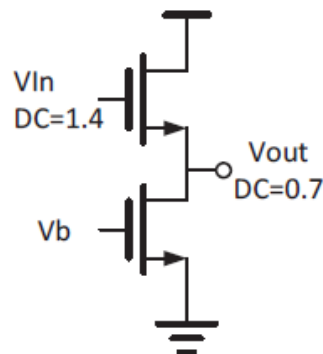


Fig.3 (b)

☆ *The following should be included in your report (a) schematic (b) HSPICE netlist (c) waveform with cursor values (d) comments.*