

2022 Analog IC Design Homework 4

due date: 06/01/2022

1. Design a differential to single-ended amplifier with $V_{dd} = 1.5V$, $C_L = 0.5pF$ as shown in Fig. 1. (45%)

 


Fig.1.

(operation point)

- (a) Please design the device size of $M_1 \sim M_4$, M_b , the input common mode voltage and V_b , to get voltage DC gain $A_v > 20 \text{ dB}$ and its bandwidth (-3dB point to DC gain) has to be larger than 5MHz. (5%)
(Please note, since M_b serves as a current source, M_b must stay in the saturation region).

- (b) Please use **.op** command to print out the small signal parameters of active devices from list file. Use **.op**'s parameters to calculate the DC gain and check your calculation and the simulation results in (a). (10%)

(frequency response)

- (c) The small signal -3dB bandwidth has to be larger than 5MHz. Please simulate and plot the frequency response of this gain stage. Use **.pz** to simulate and mark the poles/zeros on this curve. (5%)
- (d) Please use **.op** command to print out the small signal parameters of active devices from list file. Use **.op**'s parameters to calculate the output pole, mirror pole and the first zero of $V_{out}/V_{in}(s)$ frequency response. Check your calculation and the simulation results in (c). (10%)
- (e) Here we define “Bandwidth (MHz) / tail current (uA)” as figure of merit (FOM). Please try to make this FOM maximal. (5%)
- (f) Please fill the following table and discuss your design for best FOM. (10%)

| Working item | Specification | Simulation | Calculation |
|--------------------------------------|------------------------------------|------------|-------------|
| Vdd | 1.5 V | | |
| C _L | 0.5 p | | |
| Tail current (uA) | Open for design (#1) | | |
| Voltage DC gain | > 20 dB | | |
| Input common mode voltage | Open for design (V _{BS}) | | |
| Output common mode voltage | Open for design | | |
| Tail current bias voltage | Open for design (V _b) | | |
| Input size M _{1,2} | Open for design (W/L), m | | |
| PMOS size M _{3,4} | Open for design (W/L), m | | |
| Tail current MOS size M _b | Open for design (W/L), m | | |
| Bandwidth (MHz) | > 5 MHz (#2) | | |
| FOM | (#2)/(#1) | | |

★ *Tips*

You can use the following command to simulate the differential input signal, it's a VCVS

Vac in gnd ac = 1

Vicm Vicm 0 dc = ____

Eacp Vip vicm in 0 0.5

Eacn Vin vicm in 0 -0.5

.pz V(Vout) Vac

2. Design a two-stage Op amp with $V_{dd} = 1.5V$, $C_L = 1pF$ as shown in Fig. 2. (55%)

 


Fig.2.

- ★ In this design, the differential mode DC gain $> 60dB$, unity gain frequency $> 60MHz$, and phase margin $> 45^\circ$.

- (a) Operation point (10%)

- A. Please **DESIGN and LIST** your bias MOS ($M_{b1} - M_{b3}$), amplifier ($M_1 - M_6$) size, and $V_{b1} - V_{b3}$ to make the **differential mode gain at DC larger than 60dB**.

| The information of the circuit | | | |
|--------------------------------|--|----------------------------|--|
| M_{b1} | | V_{b1} | |
| M_{b2} | | V_{b2} | |
| M_{b3} | | V_{b3} | |
| $M_{1,2}$ | | Input common mode voltage | |
| $M_{3,4}$ | | Output common mode voltage | |
| $M_{5,6}$ | | | |

- B. Print out the results from **.op** command. And make sure all the devices are properly biased.
 C. Use **.tf** command to print out the voltage gain.
 D. Verify your DC gain with hand calculation.

- (b) With compensation capacitor $C_{C1,2}$ and nulling resistor $R_{C1,2}$ (20%)

- A. Please design your value of $R_{C1,2}$ and $C_{C1,2}$. Simulate and plot the frequency response (magnitude and phase) of your design in (a).

(Mark the (i) DC gain (ii) unity gain frequency, and (iii) phase margin on figure.)

- ★ Please note, your **unity gain frequency must be larger than 60MHz and phase margin must larger than 45° in this case**.

- B. Use **.pz** to simulate and mark the poles/zeros and mark them on bode plot.
 C. Verify the compensation with hand calculation.

(c) Remove $C_{C1,2}$ and $R_{C1,2}$ in Fig.2. (10%)

- A. Simulate and plot the frequency response (magnitude and phase) of your design.
(Mark the (i) DC gain (ii) unity gain frequency, and (iii) phase margin on figure.)
- B. Use **.pz** to identify the poles and zeros, and mark them on bode plot.
- C. Verify the first and second dominant poles and first RHP zeros with hand calculation.

(d) Compare the result in (b), (c) and comment what causes the difference. (15%)

(e) Please fill the following table.

| Performance Table | | |
|--|-------|--|
| V _{DD} | 1.5 V | |
| R _c , C _c | | |
| Input common mode voltage | | |
| Output common mode voltage | | |
| Open-loop performance (after compensation) | | |
| Differential mode DC gain (> 60dB) | | |
| Unity gain frequency (1pF load)(> 60MHz) | | |
| Phase margin (> 45°) | | |

★ *All device in the circuit must be in Saturation Region !!!!!*

★ *Tips*

You can use the following command to get the phase of the circuit
.probe AC Vp(Vop)

★ *The following should be included in your report (a) schematic (b) HSPICE netlist*
(c) waveform with cursor values (d) comments.